

CSL 302 Digital Logic & Computer Organization and Architecture

Aim – Basic gates using universal gates.

Name – Shravani Sandeep Raut


SE/ 48

- **Universal gates -**


- AND, OR, NOT are called basic gates as their logical operation cannot be simplified further.
- NAND and NOR are called universal gates as using only NAND or only NOR, any logic function can be implemented.

- **Implementation of NAND gate using -**


1. **NOT gate**

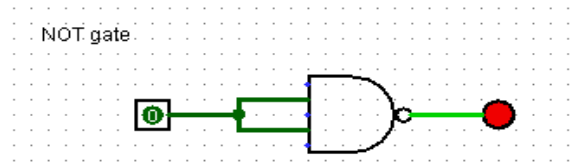


1. **AND gate**

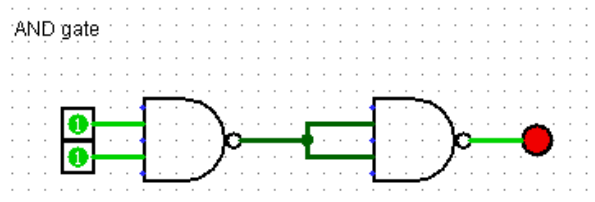


2. **OR gate**

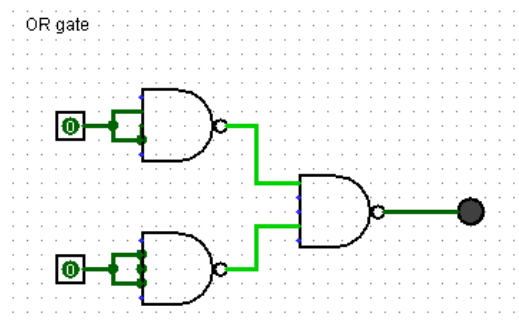

3. NOR gate

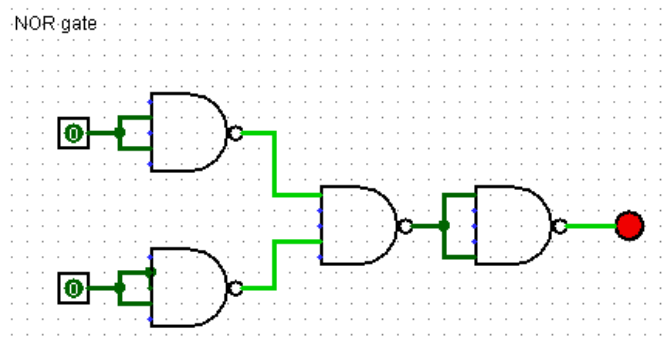


4. Ex - OR gate

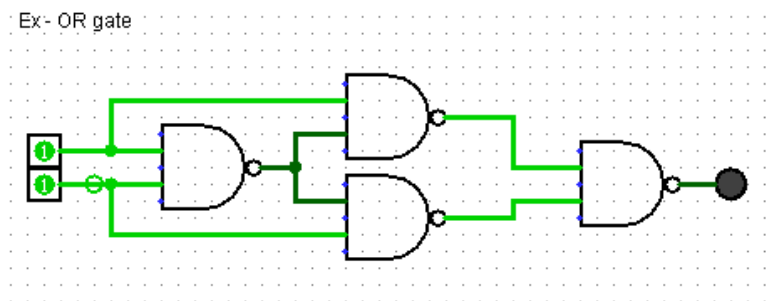


Using Logisim Software -

Implementation of NAND gate using


NOT gate

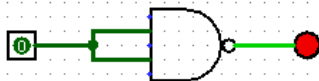


AND gate

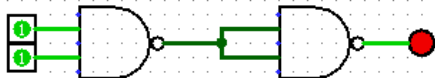


OR gate

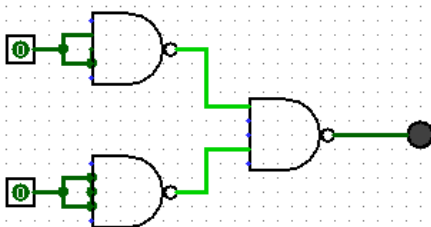

NOR gate

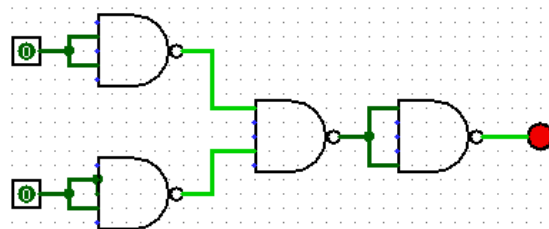


Ex - OR gate

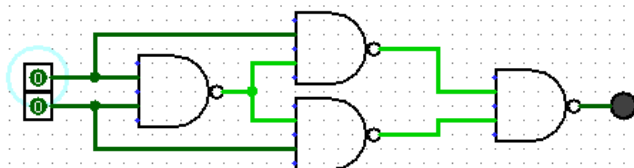


- Implementation using NOR gate


1. NOT gate

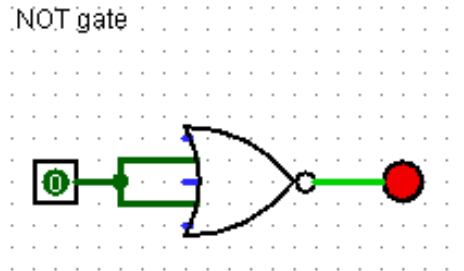


2. AND gate

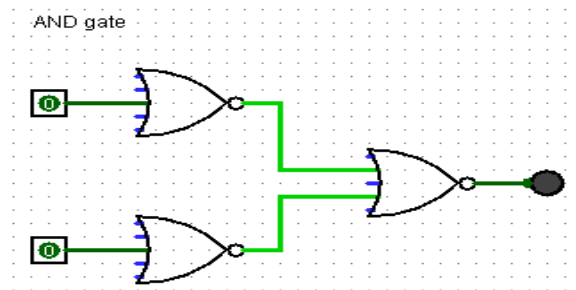


3. OR gate

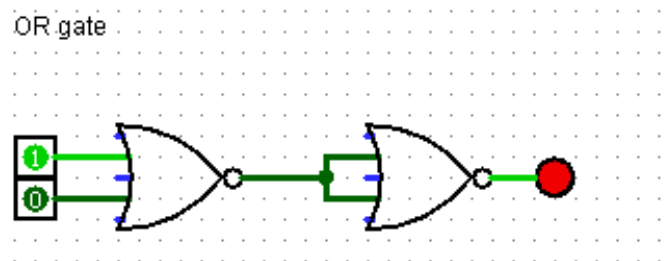

4. NAND gate

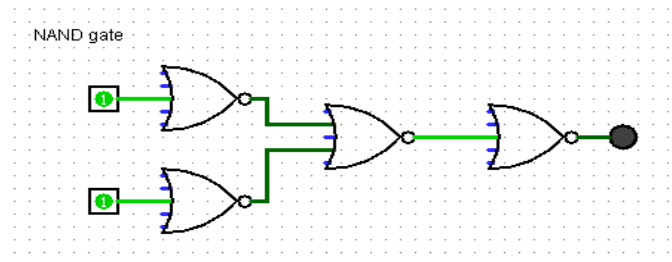


5. Ex- NOR gate

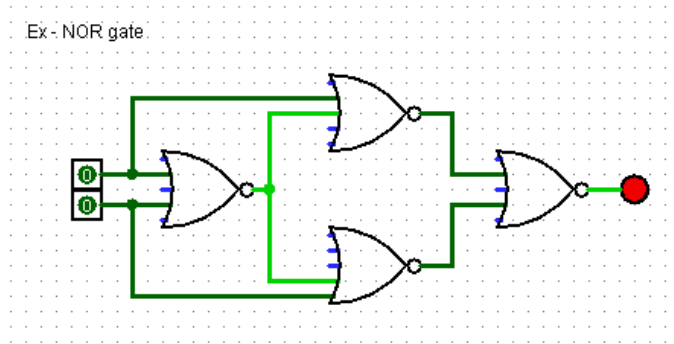


Using Logisim software -

Implementation using NOR gate


NOT gate

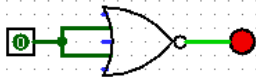


AND gate

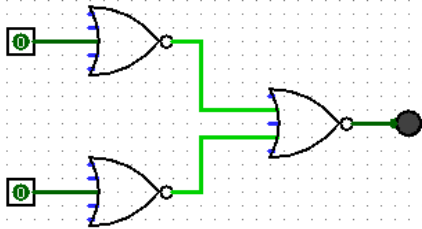

OR gate

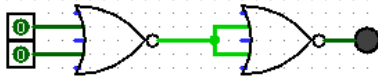

NAND gate

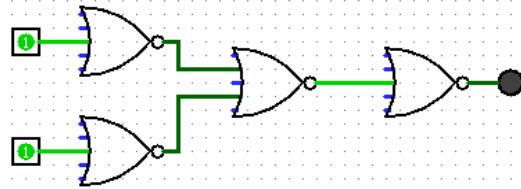

Ex - NOR gate

